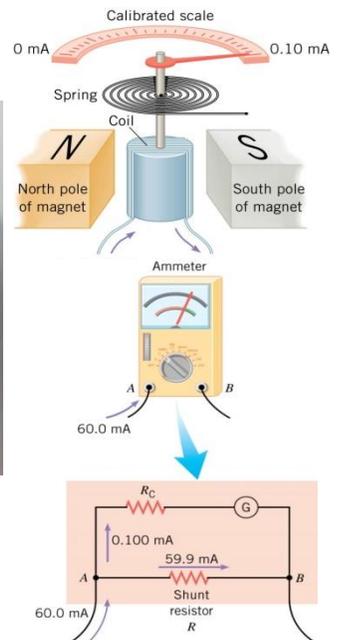


DC Voltmeters and Ammeters

- _____ (non-digital) meters
- Main component → _____

Ammeters

- Measures _____
- Inserted into _____ so _____ passes _____ it
- Connected in _____
- Coil usually measures only _____ current
- Has _____ connected in _____ to galvanometer so excess current can _____
- A _____ lets you _____ which shunt resistor is _____
- Problems with Ammeters
 - The _____ of the coil and shunt _____ add to the _____ of the circuit
 - This _____ the _____ in the circuit
 - _____ ammeter has _____ resistance
 - Real-life good _____ have _____ resistance so as only cause a _____ change in current



Voltmeters

- Connected in _____ to _____ since parallel has same _____
- The coil works just like in the _____
- Given the _____ and the _____ of the coil → _____
- To give more range, a _____ resistor is connected in _____ with the coil
- Problems with Voltmeters
 - The voltmeter takes some the _____ out of the _____
 - _____ voltmeter would have _____ resistance as to draw _____ current
 - Good voltmeter has large _____ resistance as to make the _____ draw (and voltage drop) _____



Homework

- Suppose you are using a multimeter (one designed to measure a range of voltages, currents, and resistances) to measure current in a circuit and you inadvertently leave it in a voltmeter mode. What effect will the meter have on the circuit? What would happen if you were measuring voltage but accidentally put the meter in the ammeter mode?
- Specify the points to which you could connect a voltmeter to measure the following potential differences in Figure 1: (a) the potential difference of the voltage source; (b) the potential difference across R_1 ; (c) across R_2 ; (d) across R_3 ; (e) across R_2 and R_3 . Note that there may be more than one answer to each part.
- To measure currents in Figure 1, you would replace a wire between two points with an ammeter. Specify the points between which you would place an ammeter to measure the following: (a) the total current; (b) the current flowing through R_1 ; (c) through R_2 ; (d) through R_3 . Note that there may be more than one answer to each part.
- What is the sensitivity of the galvanometer (that is, what current gives a full-scale deflection) inside a voltmeter that has a $1.00\text{-M}\Omega$ resistance on its 30.0-V scale? (OpenStax 21.42) **$30.0\ \mu\text{A}$**

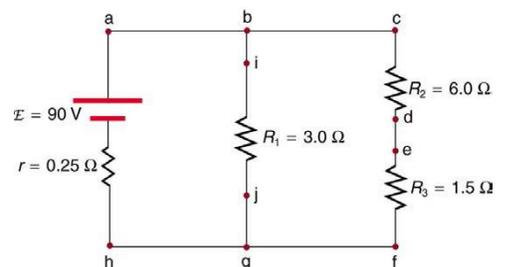


Figure 1

5. What is the sensitivity of the galvanometer (that is, what current gives a full-scale deflection) inside a voltmeter that has a $25.0\text{-k}\ \Omega$ resistance on its 100-V scale? (OpenStax 21.43) **$4.00\ \text{mA}$**
6. Find the resistance that must be placed in series with a $25.0\text{-}\Omega$ galvanometer having a $50.0\text{-}\mu\text{A}$ sensitivity to allow it to be used as a voltmeter with a 0.100-V full-scale reading. (OpenStax 21.44) **$1.98\ \text{k}\Omega$**
7. Find the resistance that must be placed in series with a $25.0\text{-}\Omega$ galvanometer having a $50.0\text{-}\mu\text{A}$ sensitivity to allow it to be used as a voltmeter with a 3000-V full-scale reading. Include a circuit diagram with your solution. (OpenStax 21.45) **$6.00 \times 10^7\ \Omega$**
8. Find the resistance that must be placed in parallel with a $25.0\text{-}\Omega$ galvanometer having a $50.0\text{-}\mu\text{A}$ sensitivity to allow it to be used as an ammeter with a 10.0-A full-scale reading. Include a circuit diagram with your solution. (OpenStax 21.46) **$1.25 \times 10^{-4}\ \Omega$**
9. Find the resistance that must be placed in parallel with a $25.0\text{-}\Omega$ galvanometer having a $50.0\text{-}\mu\text{A}$ sensitivity to allow it to be used as an ammeter with a 300-mA full-scale reading. (OpenStax 21.47) **$4.17 \times 10^{-3}\ \Omega$**