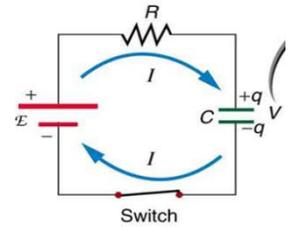


**Charging a Capacitor**

- Circuit with a \_\_\_\_\_, \_\_\_\_\_, and \_\_\_\_\_
- Initially capacitor is \_\_\_\_\_
- When battery connected current \_\_\_\_\_ to charge \_\_\_\_\_
- As charges build up, there is \_\_\_\_\_ resistance because of the \_\_\_\_\_ of the \_\_\_\_\_ on the parallel \_\_\_\_\_
- When capacitor is \_\_\_\_\_ charged, \_\_\_\_\_ current will flow



$$q = CV \left( 1 - e^{-\frac{t}{RC}} \right)$$

- $RC = \tau$  (time constant - The time required to charge the capacitor to 63.2%)
- $CV = Q$  (maximum charge)

$$V = \mathcal{E} \left( 1 - e^{-\frac{t}{RC}} \right)$$

- V is voltage across the capacitor,  $\mathcal{E}$  is emf, t is time, R is resistance of circuit, C is capacitance

**Discharging a Capacitor**

- The battery is \_\_\_\_\_
- The \_\_\_\_\_ acts like a \_\_\_\_\_ supplying \_\_\_\_\_ to the circuit

$$q = Q e^{-\frac{t}{RC}}$$


$$V = V_0 e^{-\frac{t}{RC}}$$

- Often capacitors are used to charge \_\_\_\_\_, then discharge \_\_\_\_\_ like in camera flash.
- Done by have \_\_\_\_\_ values for \_\_\_\_\_ in charging and discharging.
- Camera flashes work by charging a \_\_\_\_\_ with a \_\_\_\_\_.
  - Usually has a large time constant because \_\_\_\_\_ cannot produce charge very \_\_\_\_\_
  - The capacitor is then \_\_\_\_\_ through the \_\_\_\_\_ circuit with a \_\_\_\_\_ time constant

An uncharged capacitor and a resistor are connected in series to a battery. If  $V = 12 \text{ V}$ ,  $C = 5 \mu\text{F}$ , and  $R = 8 \times 10^5 \Omega$ . Find the time constant, max charge, max current, and charge as a function of time.


**Homework**

- Regarding the units involved in the relationship  $\tau = RC$ , verify that the units of resistance times capacitance are time, that is,  $\Omega \cdot F = s$ .
- When making an ECG measurement, it is important to measure voltage variations over small time intervals. The time is limited by the  $RC$  constant of the circuit—it is not possible to measure time variations shorter than  $RC$ . How would you manipulate  $R$  and  $C$  in the circuit to allow the necessary measurements?

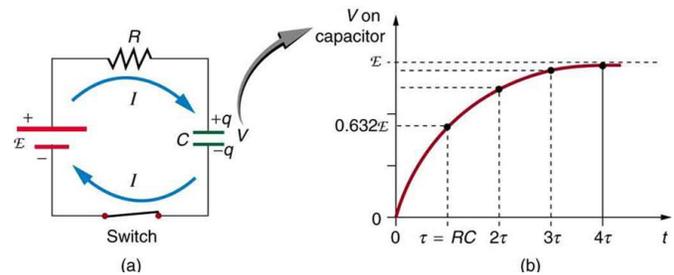
**Figure 1**

- When charging a capacitor, as discussed in conjunction with Figure 1, how long does it take for the voltage on the capacitor to reach emf? Is this a problem?
- When discharging a capacitor, as discussed in conjunction with Figure 2, how long does it take for the voltage on the capacitor to reach zero? Is this a problem?

- An electronic apparatus may have large capacitors at high voltage in the power supply section, presenting a shock hazard even when the apparatus is switched off. A “bleeder resistor” is therefore placed across such a capacitor, as shown schematically in Figure 3, to bleed the charge from it after the apparatus is off. Why must the bleeder resistance be much greater than the effective resistance of the rest of the circuit? How does this affect the time constant for discharging the capacitor?

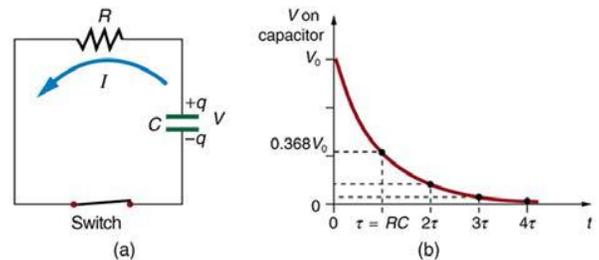**Figure 2**

- The timing device in an automobile’s intermittent wiper system is based on an  $RC$  time constant and utilizes a  $0.500\text{-}\mu\text{F}$  capacitor and a variable resistor. Over what range must  $R$  be made to vary to achieve time constants from  $2.00$  to  $15.0$  s? (OpenStax 21.63)  **$4.00$  to  $30.0$   $\text{M}\Omega$**
- A heart pacemaker fires  $72$  times a minute, each time a  $25.0\text{-nF}$  capacitor is charged (by a battery in series with a resistor) to  $0.632$  of its full voltage. What is the value of the resistance? (OpenStax 21.64)  **$3.33 \times 10^7$   $\Omega$**
- The duration of a photographic flash is related to an  $RC$  time constant, which is  $0.100$   $\mu\text{s}$  for a certain camera. (a) If the resistance of the flash lamp is  $0.0400$   $\Omega$  during discharge, what is the size of the capacitor supplying its energy? (b) What is the time constant for charging the capacitor, if the charging resistance is  $800$   $\text{k}\Omega$ ? (OpenStax 21.65)  **$2.50$   $\mu\text{F}$ ,  $2.00$  s**
- A  $500\text{-}\Omega$  resistor, an uncharged  $1.50\text{-}\mu\text{F}$  capacitor, and a  $6.16\text{-V}$  emf are connected in series. (a) What is the initial current? (b) What is the  $RC$  time constant? (c) What is the current after one time constant? (d) What is the voltage on the capacitor after one time constant? (OpenStax 21.68)  **$12.3$  mA,  $7.50 \times 10^{-4}$  s,  $4.53$  mA,  $3.89$  V**
- An ECG monitor must have an  $RC$  time constant less than  $1.00 \times 10^2$   $\mu\text{s}$  to be able to measure variations in voltage over small time intervals. (a) If the resistance of the circuit (due mostly to that of the patient’s chest) is  $1.00$   $\text{k}\Omega$ , what is the maximum capacitance of the circuit? (b) Would it be difficult in practice to limit the capacitance to less than the value found in (a)? (OpenStax 21.70)  **$1.00 \times 10^{-7}$  F, No**

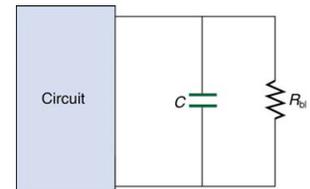**Figure 3**